

ECEN Academy

Answers for the Electrical_Problems_Set 5

Q41. What is the value of R?

A41. 10 Ω

Q42. What is the value of R?

A42. 2.4 Ω

Q43. What is the value of I?

A43. 4 A

Q44. What is the value of I1?

A44. 1 A

Q45. What is the value of I2?

A45. 3 A

Q46. What is the value of V?

A46. 4 V

Q47. What is the value of V1?

A47. 6 V

Q48. What is the value of V?

A48. 15 V

Q49. What is the value of I1?

A49. 1.5 A

Q50. What is the value of I2?

A50. 4.5 A

