

ECEN Academy

Answers for the Electrical_Problems_Set 6

Q51. What is the value of I ?

A51. 0.5 A

Q52. What is the value of V_1 ?

A52. 115 V

Q53. What is the value of V_1 ?

A53. 92 V

Q54. What is the value of V_2 ?

A54. 138 V

Q55. What is the value of I ?

A55. 0.1 A

Q56. What is the value of I ?

A56. 0.05 A

Q57. What is the value of V_1 ?

A57. 46 V

Q58. What is the value of V_2 ?

A58. 69 V

Q59. What is the value of P ?

A59. 24 W

Q60. What is the value of P ?

A60. 100 W

