

ECEN Academy

Answers for the Electrical_Problems_Set 4

Q31. What is the value of I_1 ?

A31. 5 A

Q32. What is the value of I_2 ?

A32. 2 A

Q33. What is the value of I ?

A33. 7 A

Q34. What is the value of I_2 ?

A34. .5 A

Q35. What is the value of R_2 ?

A35. 24 Ω

Q36. What is the value of V ?

A36. 4 V

Q37. What is the value of V ?

A37. 32 V

Q38. What is the value of I ?

A38. 5.01 A

Q39. What is the value of I ?

A39. 10.01 mA

Q40. What is the value of I_2 ?

A40. 1 mA (approximate)

