

ECEN Academy

Analog Electronics Set 2 Answers

Question 11: What is the V_o voltage

Answer 11: 4.3V

Question 12: What is the V_o Voltage

Answer 12: 4.3V

Question 13: What is the V_o Voltage

Answer 13: 0.7V

Question 14: What is V_o Voltage

Answer 14: 0.7V

Question 15: What is V_o Voltage

Answer 15 : 0.7V

Question 16: What is V_o Voltage

Answer 16: 2.7V

Question 17: What is V_o Voltage

Answer 17 : 0V

Question 18: What is V_o Voltage

Answer 18 : 5V

Question 19: What is the V_o Voltage

Answer 19 : 0V

Question 20: What is the V_o Voltage

Answer 20 : 5V