

ECEN Academy

Answers for the Electrical_Problems_Set 3

Q21. What is the value of Current?

A21. 1A

Q22. What is the value of Voltage V2?

A22. 2V

Q23. What is the value of Voltage V1?

A23. 3V

Q24. What is the value of Current?

A24. 1A

Q25. What is the value of Resistance?

A25. 6Ohm

Q26. What is the value of Voltage?

A26. 20V

Q27. What is the value of Current?

A27. 14V

Q28. What is the value of Resistance?

A28. 3Ohm

Q29. What is the value of Voltage?

A29. 18V

Q30. What is the value of Voltage?

A30. 12V