

ECEN Academy

Answers for the Electrical_Problems_Set 7

Q61. What is the value of I ?

A61. 0.5 A

Q62. What is the value of V_1 ?

A62. 115 V

Q63. What is the value of I_1 ?

A63. 0.5 A

Q64. What is the value of I ?

A64. 1 A

Q65. What is the value of I_1 ?

A65. 0.5 A

Q66. What is the value of V_1 ?

A66. 115 V

Q67. What is the value of I ?

A67. 0.22 A

Q8. What is the value of I_1 ?

A8. 0.1 A

Q69. What is the value of V_1 ?

A69. 92 V

Q70. What is the value of V_d ?

A70. 96 V

